

8086 microprocessor characteristics:

- It contains 20 bit address bus.
- It contains 16-bit data bus, therefore 8086 is called as **16-bit microprocessor**.
- It is 2-stage pipelined processor. It can prefetch 6 bytes from memory and store into queue to increase the speed of the execution.
- It's control bus carries signals for executing operations such as read ,write etc.
- It has Memory Banks. 2 banks of 512KB each. These banks are called as lower Bank (even) and higher Bank (odd).
- In 8086 the entire memory is divided into four memory segments which are code ,stack, data and extra segment.
- 8086 has 16 bit IO address.
- It has 256 interrupts.

8086 has two operating Modes:

1. Minimum mode
2. Maximum mode

Minimum mode:

- In this 8086 is the only processor in the system . In a minimum mode 8086 system.
- 8086 is operated in minimum mode when MN/MX' pin to logic 1.
- In this mode, all the control signals are given out by the 8086 itself.


Minimum mode configuration of 8086 microprocessor (Min mode)

Overview:

- The 8086 microprocessor operates in minimum mode when MN/MX' = 1.
- In minimum mode, 8086 is the only processor in the system which provides all the control signals which are needed for memory operations and I/O interfacing.
- Here the circuit is simple but it does not support multiprocessing.
- The other components which are transceivers, latches, 8284 clock generator, 74138 decoder, memory and i/o devices are also present in the system.
- The address bus of 8086 is 20 bits long. By this we can access 2^{20} byte memory i.e. 1MB. Out of 20 bits, 16 bits A_0 to A_{15} (or 16 lines) are multiplexed with a data bus. By multiplexing, it means they will act as address lines during the first T state of the machine cycle and in the rest, they act as data lines. A_{16} to A_{19} are multiplexed S_3 to S_6 and BHE' is multiplexed with S_7 .

Control signals provided by 8086 for memory operations and i/o interfacing:

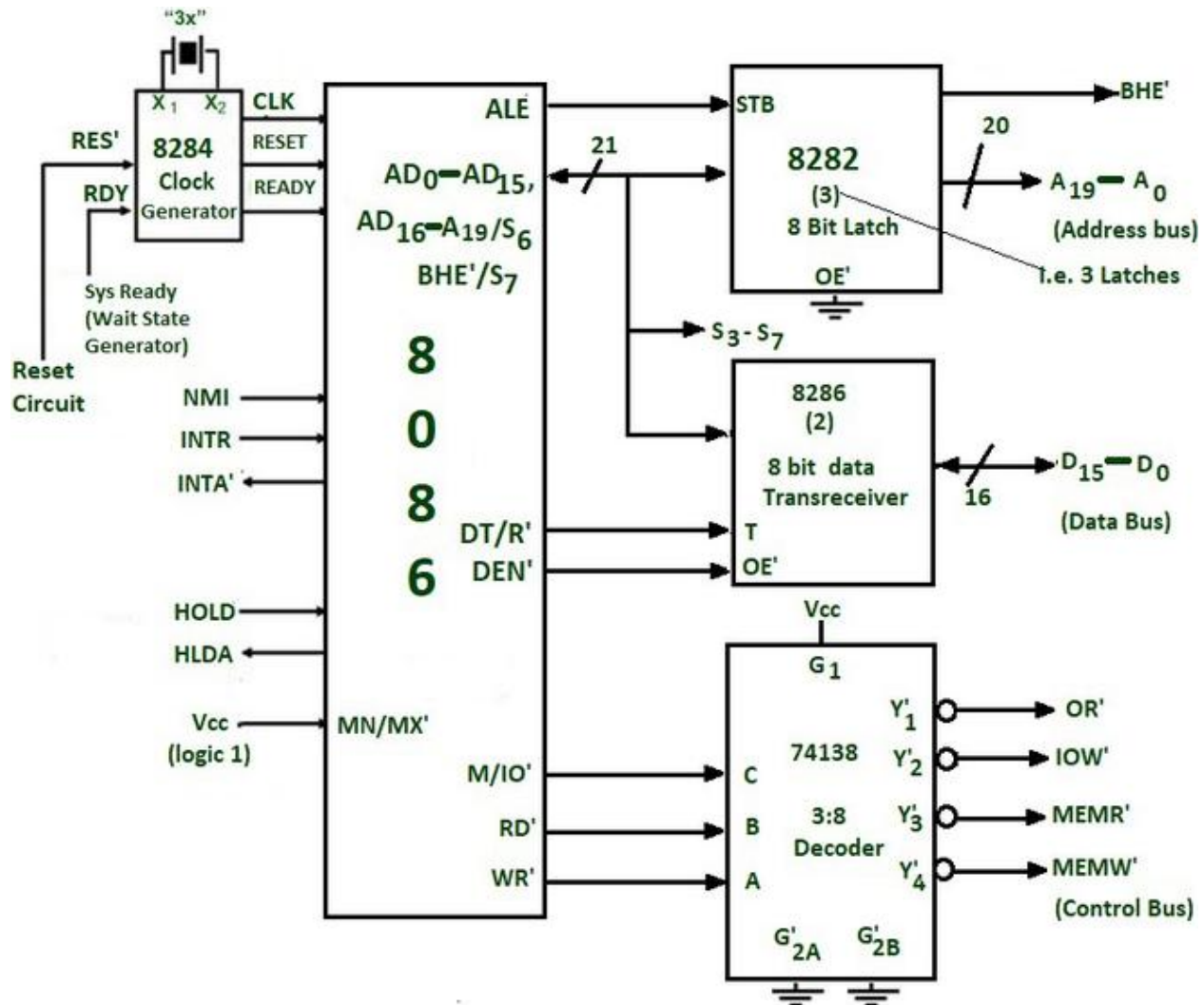They are used to identifying whether the bus is carrying a valid address or not, in which direction data is needed to be transferred over the bus, when there is valid write data on the data bus and when to put read data on the system bus. Therefore, their sequence pattern makes all the operations successful in a particular machine cycle.



8282 (8 bits) latch:

The latches are buffered D FF. They are used to separate the valid address from the multiplexed Address/data bus by using the control signal ALE , which is connected to strobe (STB) of 8282. The ALE is active high signal. Here three such latches are required because the address is 20 bits.

8286 (8 bits) transceivers:

They are bidirectional buffers and also known as data amplifiers. They are used

to separate the valid data from multiplexed add/data bus. Two such transceivers are needed because the data bus is 16 bits long. 8286 is connected to DT/R' and DEN' signals. They are enabled through the DEN' signal. The direction of data on the data bus is controlled by the DT/R' signal. DT/R' is connected to T and DEN' is connected to OE'.

DEN'	DT/R'	Action
1	X (don't care)	Transreceiver is disabled
0	0	Receiver data
0	1	Transmit data

- 8284 clock generator is used to provide the clock.
- M/IO' = 1, then I/O transfer is performed over the bus and when M/IO' = 0, then I/O operation is performed.
- The signals RD' and write WR' are used to identify whether a read bus cycle or a write bus cycle is performing. When WR' = 0, then it indicates that valid output data on the data bus.
- RD' indicates that the 8086 is performing a read data or instruction fetch process is occurring. During read operations, one other control signal is also used, which is DEN (data enable) and it indicates the external devices when they should put data on the bus.
- Control signals for all operations are generated by decoding M/IO', RD', WR'. They are decoded by 74138 3:8 decoder.

M/IO'	RD'	WR'	Action
1	0	1	Memory Read
1	1	0	Memory Write
0	0	1	I/O Read
0	1	0	I/O Write


- **INTR and INTA :**
When INTR = 1, then there is an interrupt to 8086 by other devices for their service. When INTA' = 0, then it indicates that the processor is ready to service them.

- The bus request is made by other devices using the HOLD signal and the processor acknowledges them using the HLDA output signal.

Timing diagram :

The working of min mode can be easily understood by timing diagrams.


- All processors bus cycle is of at least 4 T-states(T_1, T_2, T_3, T_4). The address is given by processor in the T_1 state. It is available on the bus for **one T-state**.
- In T_2 , the bus is tristated for changing the direction of the bus(in the case of a data read cycle.)
- The data transfer takes place between T_3 and T_4 .
- If the addressed device is slower, then the wait state is inserted between T_3 and T_4 .

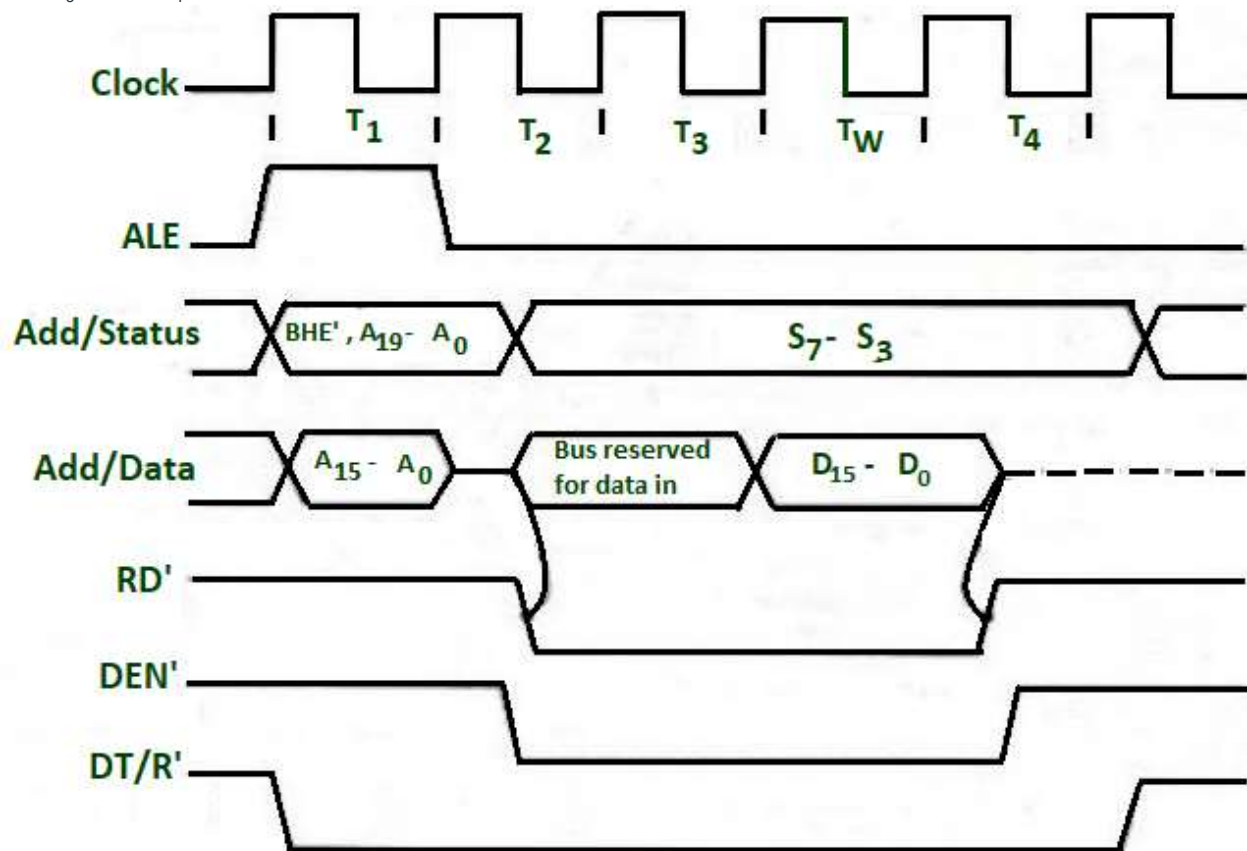

Opcode fetch or read timing diagram


- At T_1 state $ALE = 1$, this indicates that a valid address is latched on the address bus and also $M / IO' = 1$, which indicates the memory operation is in progress.
- In T_2 , the address is removed from the local bus and is sent to the addressed device. Then the bus is tristated.
- When $RD' = 0$, the valid data is present on the data bus.

- During T_2 $DEN' = 0$, which enables transceivers and $DT/R' = 0$, which indicates that the data is received.
- During T_3 , data is put on the data bus and the processor reads it.
- The output device makes the READY line high. This means the output device has performed the data transfer process. When the processor makes the read signal to 1, then the output device will again tristate its bus drivers.

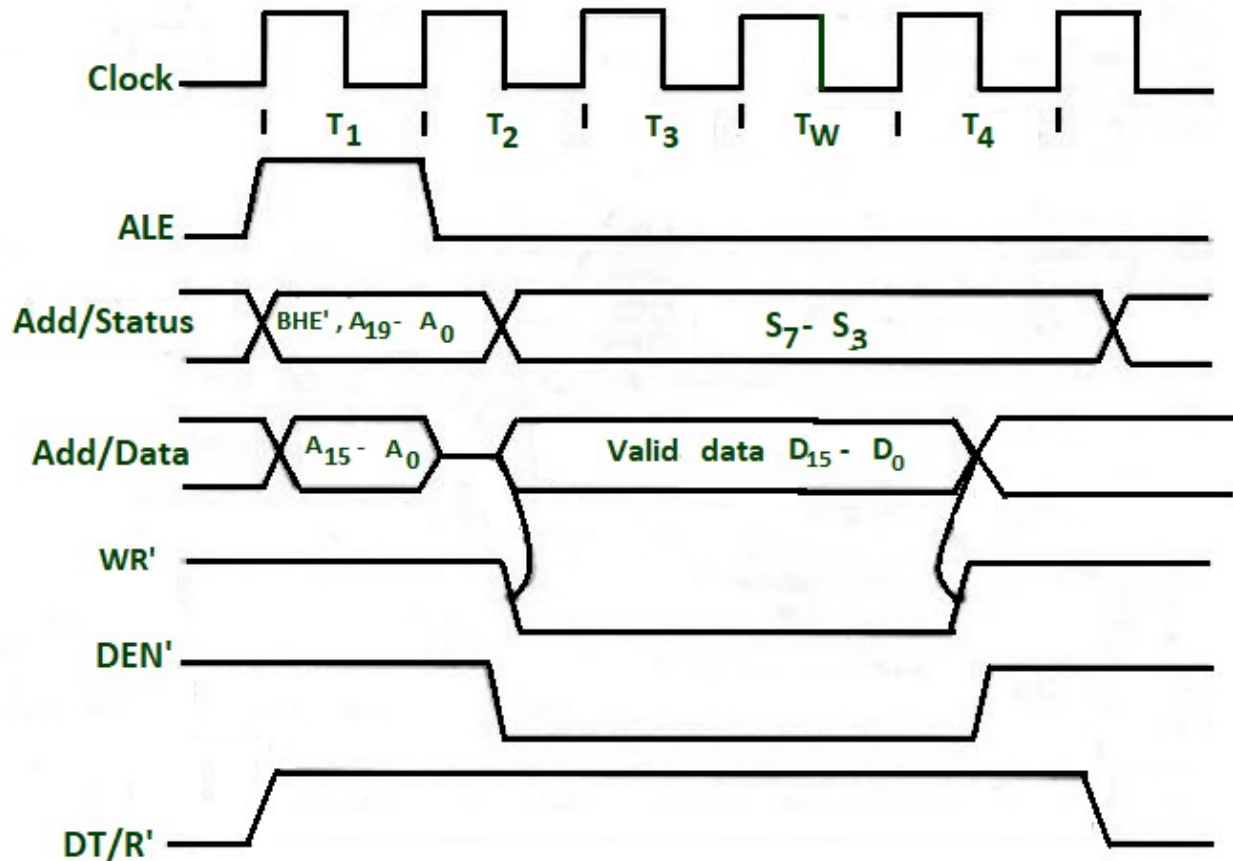

Write memory cycle

- At T_1 state $ALE = 1$, this indicates that a valid address is latched on the address bus and also $M / IO' = 1$, which indicates the memory operation is in progress.
- In T_2 , the address is removed from the local bus and is sent to the addressed device. Then the bus is tristated.
- When $RD' = 0$, the valid data is present on the data bus.
- During T_2 $DEN' = 0$, which enables transceivers and $DT/R' = 0$, which indicates that the data is received.
- During T_3 , data is put on the data bus and the processor reads it.
- The output device makes the READY line high. This means the output device has performed the data transfer process. When the processor makes the read signal to 1, then the output device will again tristate its bus drivers.

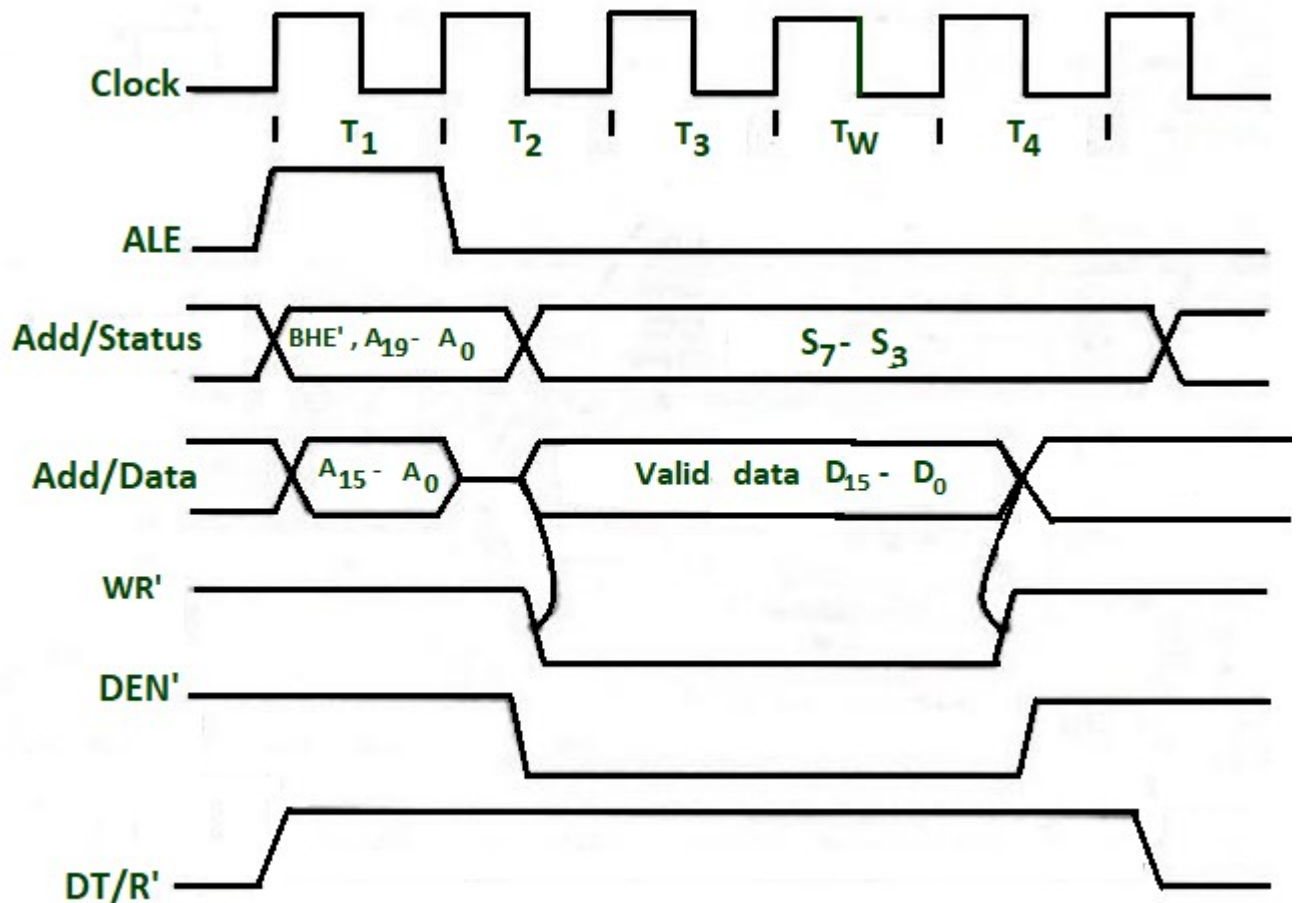

Write memory cycle


- At T_1 state $ALE = 1$, this indicates that a valid address is latched on the address bus and also $M / IO' = 1$, which indicates the memory operation is in progress.
- In T_2 , the processor sends the data to be written to the addressed location.
- The data is buffered on the bus until the middle of T_4 state.
- The $WR' = 0$ becomes at the beginning of T_2 .
- The BHE' and A_0 signals are used to select the byte or bytes of memory or I/O word.
- During T_2 $DEN' = 0$, which enables, transceivers and $DT/R' = 1$, which indicates that the data is transferred by the processor to the addressed device.

All kinds of memory and i/o operations are performed using the decoding of M/IO' and RD' WR' as shown in the table above.

Maximum mode configuration of 8086 microprocessor (Max mode)

Maximum mode:

- In this we can connect more processors to 8086 (8087/8089).
- 8086 max mode is basically for implementation of allocation of global resources and passing bus control to other coprocessor(i.e. second processor in the system), because two processors can not access system bus at same instant.
- All processors execute their own program.
- The resources which are common to all processors are known as global resources.
- The resources which are allocated to a particular processor are known as local or private resources.

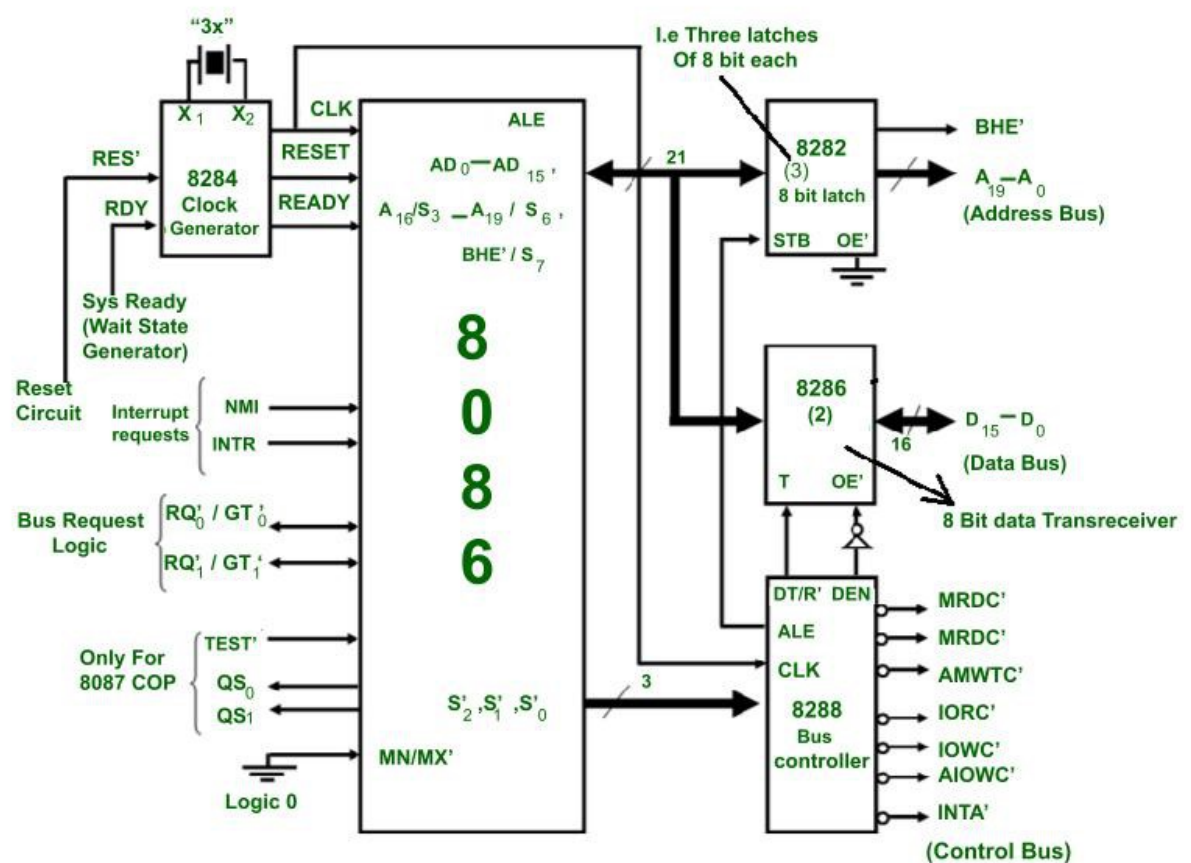

Maximum mode circuit

Circuit explanation:

- When $MN/\overline{MX}' = 0$, 8086 works in max mode.
- Clock is provided by **8284 clock generator**.
- **8288 bus controller**- Address from the address bus is latched into 8282 8-bit latch. Three such latches are required because **address bus is 20 bit**. The ALE(Address latch enable) is connected to STB(Strobe) of the latch. **The ALE for latch is given by 8288 bus controller.**
- The data bus is operated through 8286 8-bit transceiver. Two such transceivers are required, because **data bus is 16-bit**. The transceivers are enabled the DEN signal, while the direction of data is controlled by the DT/R signal. DEN is connected to \overline{OE}' and $\overline{DT}/\overline{R}'$ is connected to T. **Both DEN and $\overline{DT}/\overline{R}'$ are given by 8288 bus controller.**

DEN (Of 8288)	DT/ R'	Action
0	X	Transceiver is disabled
1	0	Receive data
1	1	Transmit data

- **Control signals for all operations are generated by decoding S'_2 , S'_1 and S'_0 using 8288 bus controller.**

S'_2	S'_1	S'_0	Processor State (What the μP wants to do)	8288 Active Output (What Control signal should 8288 generate)
0	0	0	Interrupt Acknowledge	\overline{INTA}'
0	0	1	Read I/O Port	\overline{IORC}'
0	1	0	Write I/O Port	\overline{IOWC}' and \overline{AIOWC}'
0	1	1	Halt	None
1	0	0	Instruction Fetch	\overline{MRDC}'
1	0	1	Memory Read	\overline{MRDC}'
1	1	0	Memory Write	\overline{MWTC}' and \overline{AMWTC}'
1	1	1	Inactive	None

- Bus request is done using RQ' / GT' lines interfaced with 8086. RQ₀/GT₀ has more priority than RQ₁/GT₁.
- INTA' is given by 8288, in response to an interrupt on INTR line of 8086.
- In max mode, the advanced write signals get enabled one T-state in advance as compared to normal write signals. This gives slower devices more time to get ready to accept the data, therefore it reduces the number of cycles.

Advantages of max mode of 8086:

- It helps to interface more devices like 8087. This interface is also called a **closely coupled co-Processor configuration**. In this 8086 is called as the host and 8087 as Co-processor.
- It supports multiprocessing, Therefore it helps to increase the efficiency.
- The 8087 was the first floating-point coprocessor for the 8086 series of microprocessors. The purpose of the 8087 was to increase calculations for floating point operations, such as add, sub, multiply, divide, and square root.

Disadvantages of max mode over min mode :

- It has more complex circuit than min mode.

Applications of 8086:

- Microcomputer are built using 8086. **For example** : IBM PC, used the Intel 8088, a version of the 8086 with 8-bit data bus.
- It is used in calculators.
- It is used for control purposes like in traffic signals(uses micro controllers which are nothing but contains **one or more CPUs along with memory and programmable i/o peripherals**).